

Topic 18

Alternating Current

- 1 A sinusoidal current flowing in a $10\ \Omega$ resistor varies with time according to the equation $I = 1.2 \sin(100\pi t)$. Calculate the instantaneous current and the instantaneous power dissipated at

- (a) $t = 0.005\text{ s}$

$$I = 1.2 \sin(100\pi \times 0.005) = 1.2\text{ A}$$

$$P = I^2 R = 1.2^2 \times 10 = 14.4\text{ W}$$

- (b) $t = 0.010\text{ s}$

$$I = 1.2 \sin(100\pi \times 0.010) = 0\text{ A}$$

$$P = 0\text{ W}$$

- (c) $t = 0.018\text{ s}$

$$I = 1.2 \sin(100\pi \times 0.018) = -0.705\text{ A}$$

$$P = I^2 R = (-0.705)^2 \times 10 = 4.98\text{ W}$$

- 2 Determine the r.m.s. current in each case.

- (a) A sinusoidal current of peak value 2.0 A .

$$\text{For a sinusoidal current, } I_{r.m.s.} = \frac{I_0}{\sqrt{2}} = \frac{2}{\sqrt{2}} = 1.41\text{ A}$$

- (b) A full-wave rectified sinusoidal current of peak value 3.0 A .



When a full-wave rectified sinusoidal current is squared, the power dissipated would be similar to the that of the regular sinusoidal current.

$$\text{Hence, } I_{r.m.s.} = \frac{I_0}{\sqrt{2}} = \frac{3}{\sqrt{2}} = 2.12\text{ A}$$

- (c) A square-wave current with a frequency of 1 Hz which is 0.1 A for one half cycle and -0.1 A for the next half cycle.

I^2 would yield a constant value of 0.01 A^2 . Hence $\langle I^2 \rangle = 0.01\text{ A}^2$ and $I_{rms} = 0.1\text{ A}$.

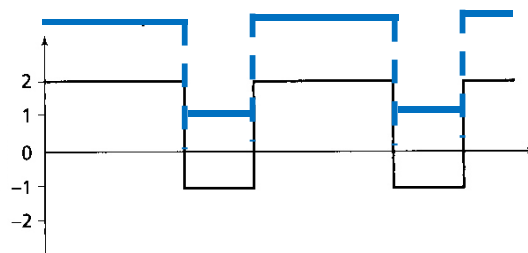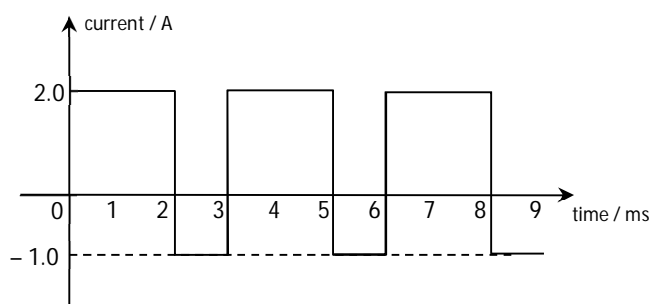- (d) An uneven square wave current as shown below.



$$\langle I^2 \rangle = \frac{\int_0^T I^2 dt}{T} = \frac{4(2) + 1(1)}{3} = 3.0\text{ A}^2$$

$$\therefore I_{rms} = \sqrt{\langle I^2 \rangle} = 1.73\text{ A}$$

- 3 An alternating current of r.m.s. value 2 A and a steady direct current I flowing through identical resistors dissipate heat at equal rates. Determine the value of current I .

Since the r.m.s. value of an a.c. is the value of a steady d.c. which will dissipate energy at the same rate as the mean power dissipated by an a.c. in a given resistor, the value of I is 2 A.

- 4 A steady current I dissipates power P in a variable resistor. The resistance has to be halved to obtain the same power when a sinusoidal alternating current is used. Determine the r.m.s. value of the alternating current in terms of I .

$$P_{dc} = I^2 R \text{ and } P_{ac} = I_{r.m.s.}^2 \frac{R}{2}$$

Since $P_{dc} = P_{ac}$

$$I^2 R = I_{r.m.s.}^2 \frac{R}{2}$$

$$I_{r.m.s.} = \sqrt{2} I$$

- 5 A sinusoidal current described by the equation $I = 9.0 \sin \omega t$ flows through a $12.0 \, \Omega$ resistor. Calculate

- (a) the r.m.s. value of the current through and potential difference across the resistor.

$$I_o = 9.0 \text{ A}$$

$$\text{For a sinusoidal current, } I_{r.m.s.} = \frac{I_o}{\sqrt{2}} = \frac{9.0}{\sqrt{2}} = 6.36 \text{ A}$$

$$V_{r.m.s.} = I_{r.m.s.} R = 6.36 \times 12 = 76.4 \text{ V}$$

- (b) the maximum instantaneous power dissipated in the resistor.

$$P_o = I_o^2 R = 9^2 \times 12 = 972 \text{ W}$$

- (c) the mean power dissipated in the resistor.


$$P_{mean} = I_{r.m.s.}^2 R = 6.36^2 \times 12 = 486 \text{ W}$$

- 6 An audio amplifier, represented by an a.c. source and the resistor R delivers alternating voltages at audio frequencies to the speaker. If the source puts out an r.m.s. alternating p.d. of 15 V, resistance R is $8.20 \, \Omega$ and the speaker is equivalent to a resistance of $10.4 \, \Omega$, calculate the average power delivered to the speaker.

By potential divider principle,

$$V_{speaker (r.m.s.)} = \frac{R_{speaker}}{R_{total}} V_{total (r.m.s.)} = \frac{10.4}{10.4 + 8.2} (15) = 8.39 \text{ V}$$
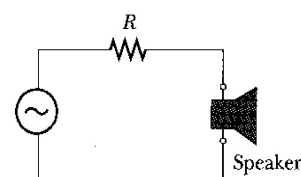
$$\langle P \rangle = \frac{V_{speaker (r.m.s.)}^2}{R_{speaker}} = \frac{8.39^2}{10.4} = 6.76 \text{ W}$$



- 7 (a) A power station generates 100 kW of power which is transmitted at a potential difference of 10 kV. Given that the connecting cables have a total resistance of 20 Ω , determine the turn ratio required for an ideal step-down transformer to bring electrical energy to the home at 240 V.

$$\text{Current through transmission cables } I_{\text{cable}} = \frac{P_{\text{transmitted}}}{V_{\text{transmission}}} = \frac{100 \times 10^3}{10 \times 10^3} = 10 \text{ A}$$

$$\text{Potential difference across transmission cable } V_{\text{cable}} = I_{\text{cable}} R = 10 \times 20 = 200 \text{ V}$$

$$\text{Potential difference at step-down transformer} = 10 \times 10^3 - 200 = 9800 \text{ V}$$

$$\text{Hence turn ratio, } \frac{N_p}{N_s} = \frac{9800}{240} = \frac{245}{6}$$

- (b) Explain why, for the efficient transmission of electrical energy, it is necessary to


- (i) use an alternating supply and

The process of stepping up (or down) utilizes the concept of electromagnetic induction which requires a changing magnetic linkage linking the secondary coil. This means that a changing magnetic flux has to be produced at the primary coil, which can only be achieved when an alternating supply is used.

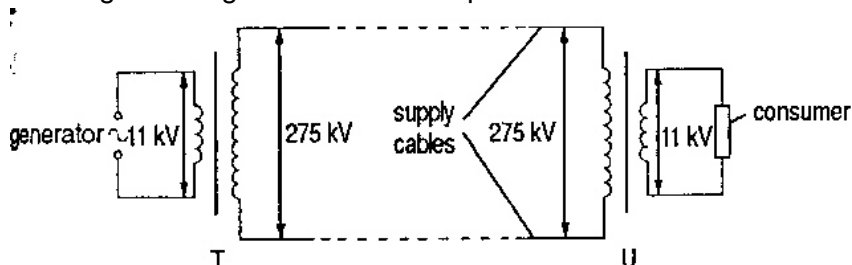- (ii) transmit at high voltage.

When electrical energy is transmitted at high voltage, the transmission current can be reduced, which will result in less power loss through the transmission cables.

- 8 Electrical power of 4400 kW is supplied to an industrial consumer at a considerable distance from a generating station. This is represented below.



In order to do this, the electricity supply company makes use of a circuit containing two transformers T and U. The transformers can be considered to be ideal and the supply cables to have negligible resistance.

- (a) The power is generated at 11 kV r.m.s. and is supplied to the consumer at 11 kV r.m.s. Calculate, for the current supplied to the consumer, its

- (i) r.m.s. value, and

$$I_{r.m.s.} = \frac{P}{V_{r.m.s.}} = \frac{4400 \times 10^3}{11 \times 10^3} = 400 \text{ A}$$

- (ii) peak value.

$$\text{For a sinusoidal current, } I_o = I_{r.m.s.} \sqrt{2} = 400 \sqrt{2} = 566 \text{ A}$$

(b) There is a potential difference of 275 kV r.m.s. between the supply cables. Calculate

(i) the ratio $\frac{N_s}{N_p}$ for each transformer

For transformer T, $\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{275}{11} = 25$

For transformer U, $\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{11}{275} = \frac{1}{25}$


(ii) the r.m.s. value of current in the supply cables

$$I_{r.m.s.} = \frac{P}{V_{r.m.s.}} = \frac{4400 \times 10^3}{275 \times 10^3} = 16 \text{ A}$$

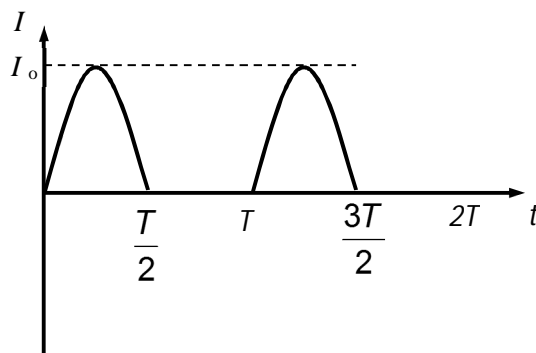
(c) Explain why, when the resistance of the supply cables cannot be neglected, this arrangement is preferable to a system which generates and transmits the power at the same voltage of 11 kV r.m.s.

If there is resistance in the supply cables, there would be power loss (I^2R) when transmitting electrical energy across the cables. With a step-up and step-down transformer, the electrical energy would be transmitted at a current lower than 400 A which would result in a much smaller power loss.

9 Determine the r.m.s. current I_{rms} , in terms of its peak current I_o , for a half-wave rectified sinusoidal current as shown below.



Squaring the current:

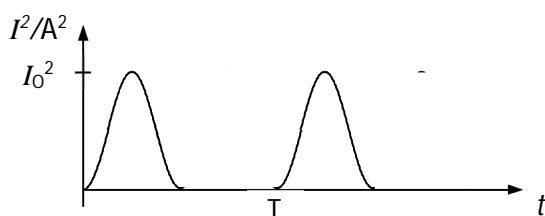

Hence, for half-wave rectification, $\langle I^2 \rangle = \frac{1}{4} I_o^2 \Rightarrow I_{rms} = \frac{1}{2} I_o$

Answer Key

- 1 (a) 1.2 A, 14.4 W (b) 0 A, 0 W (c) -0.705 A, 4.98 W
- 2 (a) 1.41 A (b) 2.12 A (c) 0.1 A (d) 1.73 A
- 3 2 A
- 4 $\sqrt{2}I$
- 5 (a) 6.4 A, 76.4 V (b) 972 W (c) 486 W
- 6 6.76 W
- 7 (a) 245:6
- 8 (a)(i) 400 A (ii) 566 A (b)(i) T:25, U: $\frac{1}{25}$ (ii) $I_{\text{rms}}=16$ A
- 9 $I_o / 2$