


# Design and Technology 7059/1

## Topic on Electronics

- 1) An electronic system has;
  - Input; for gathering information.
  - Process; decide what to do with information
  - Output; involves with switching device on/off.
- 2) Feedback – in a system with feedback, the output is fed back to the input, and depending on the output, the input is adjusted so as to reach a steady-state.
  - Open-loop control system;



- Closed-loop control system;

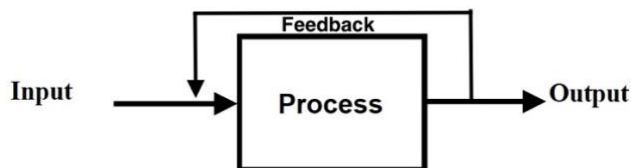

- 3) Conductors and Insulators
  - Electrical conductor; material that allows electricity to flow through easily.
  - Electrical insulator; material that electricity cannot flow through.
  - Semi-conductor; electricity can flow through them, but with difficulty.
- 4) Power Supply
  - 4a) Mains power supply has alternating current.
    - **Advantages**; It is more cost-effective and easy to transmit large amounts of power over large distances.

4b) Most common source of power is the **battery**. Batteries have a positive and negative terminal and it has potential difference (concept linkage w/ Physics, topic of 'Current of Electricity').

- Potential difference is measured in volts (V)
- Batteries in series – add voltage of batteries together to get the total voltage/electromotive force of the source. (Concept linkage w/ Physics, topic of 'DC Circuits')
- Batteries in parallel – total voltage is same as of individual battery.
- **Advantage of Batteries;** portable, generally of lower power.
- **Safety;** Never short circuit a battery, never break open a battery due to presence of corrosive chemicals, never throw batteries into a fire due to explosive potential.

4c) Photovoltaic cells/ Solar panels – converts light energy into electricity using semi-conductors.

- Generally environmentally-friendly

## 5) Electric Current and Electrical Power

5a) **Electrical Current** is the rate of charge flow per unit time.

- Measured in Amperes (A)

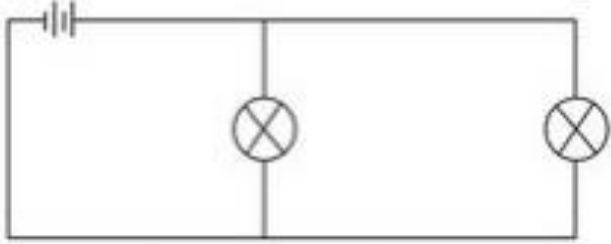

5b) **Power** is the rate of energy change.

- Measured in Watts (W)
- $Power (P) = Current (I) \times Voltage (V)$

## 6) Multimeter



- To measure current, a Ammeter is used. It must be connected in series with the circuit.
- To measure voltage, a voltmeter is used. It must be connected parallel with the circuit.

## 7) Circuits

Parralel	Series
 <p>Parallel Circuit</p>	 <p>Series Circuit</p>
<p>If resistance of the different paths in a parallel circuit is the same, current flow will be split equally amongst the separate paths. If resistance of the different paths in a parallel circuit are different, current flow will be higher in the path of lowest resistance.</p>	<p>Current is the same at any point in a circuit.</p> <p>(Physics-based explanation; At any point in the circuit, the same amount of charges flow through it. Hence, current flow is the same at any point in a parallel circuit.)</p>
<p>The potential difference of each path in the parallel circuit is equal to the electromotive force of the source.</p>	<p>The total potential difference of all the components is equivalent to the electromotive force of the source.</p>




## 8) Switches

- Switches are used to make or break a circuit.

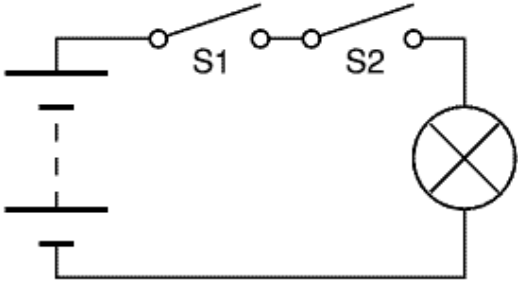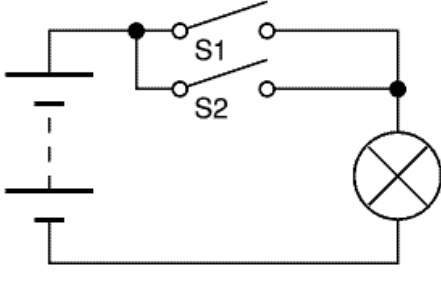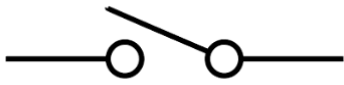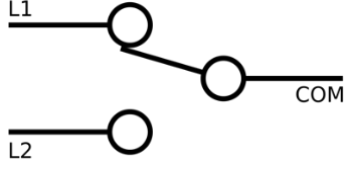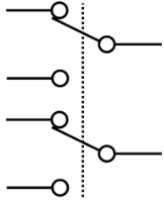
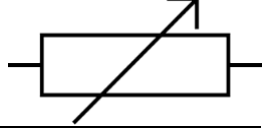
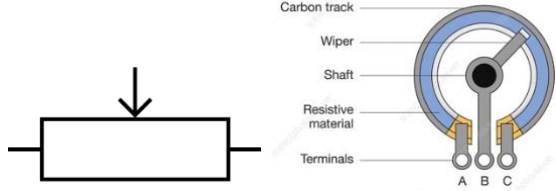

Connecting switches in series	Connecting switches in parallel
	
<p>All switches must be closed before current will flow.</p>	<p>Current will flow when any switch is closed.</p>
<p>May be used for safety reasons. E.g ovens only work when door is closed and main switch is on.</p>	<p>May be used for ease of operation. E.g. buses; pressing of any switch alerts the driver.</p>

## 8b) Types of switches

Type	Symbol	Application
------	--------	-------------

SPST (Single-pole, single-throw)		Two contacts. Simple on-and-off switch.
SPDT (Single-pole, double throw)		Three contacts. Can operate two parts of a circuit.
DPDT (Double-pole, double throw)		Six contacts. A pair of on-on switches which operate in a synchronized fashion. Can operate two different circuits at once.

### 8c) Diode, Potentiometer, Capacitors


Diode		Controls flow of current. Allows current to flow in one direction only.
Variable resistor		Used to control current.
Potentiometer		Can work as a variable resistor or as a voltage divider. To use as a variable resistor, only two pins are used. To use as a potential divider, all three pins are used.
Capacitors		Stores electrical charge. When connected to a battery, current flows into it, causing it to 'light up'. The amount of charge a capacitor can store is called capacitance. The higher the capacitance, the more charge it can store.

### 9) Transistors


- NPN Transistors are semiconductor devices used to amplify and switch electronic signals and power. It acts as a automatic switch and transistor amplifier.
- There are 3 terminals for connection to an external circuit.
- The base controls the current that flows between the collector and the emitter.
- When no current flows through the base of the transistor, the transistor is 'switched off'.
- When a small current flows into the base, the transistor

; Switches 'on', allowing a current to flow from the collector to the emitter.

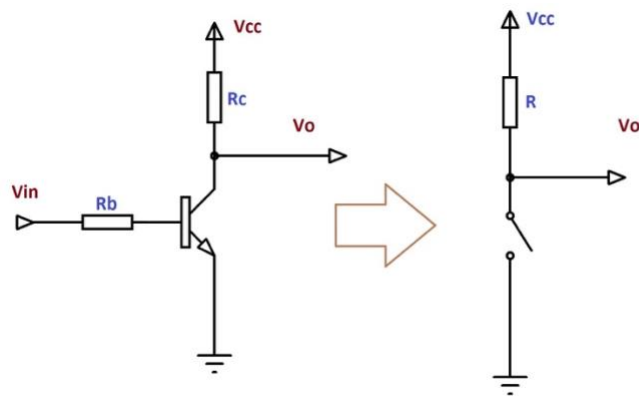; Amplifies the input current to a higher-output circuit.



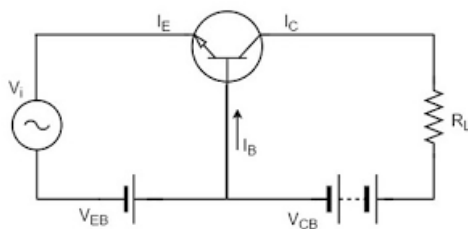- Diagram above represents the usage of transistors as a switch.




- Diagram above represents the usage of transistors as an amplifier.
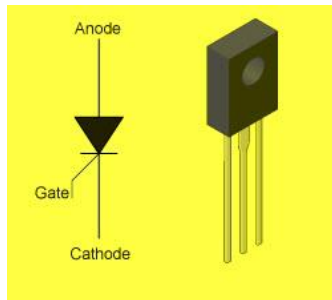
#### 10) Thyristor.

- An electronic component w/ 3 leads; anode (+), cathode (-), and gate.
- Output remains switched on once triggered until manually reset.
- The gate controls the current that flows btwn/ the anode and the cathode.
- When no current flows into the gate, the thyristor is 'off'.

- When a small current flows into the gate, the thyristor switches 'on', allowing a current to flow between the anode and cathode.
- Once triggered, it remains on even w/ no current flowing through the gate.



### 11) Resistor

- Resistors restrict current flow in a circuit.
- It is used to protect components from damage due to excessive currents in the circuit.
- Resistors have no polarity. [Can be connect either-way around].
- Resistance is measured using Ohms /  $\Omega$

Resistors are colour-coded w/ colour bands to show their values.

; The first band gives the first digit and the second band gives the second digit.

; Third band is the multiplier

; Fourth band shows the tolerance of the resistor.

	1 <sup>st</sup> digit	2 <sup>nd</sup> digit	3 <sup>rd</sup> digit	multiply	tolerance	TCR (ppm/K)
Black	0	0	0	1	1% (F)	100
Brown	1	1	1	10	2% (G)	50
Red	2	2	2	100		15
Orange	3	3	3	1K		25
Yellow	4	4	4	10K		
Green	5	5	5	100K	0.5% (D)	
Blue	6	6	6	1M	0.25% (C)	10
Violet	7	7	7	10M	0.1% (B)	5
Gray	8	8	8	100M	0.05% (A)	
White	9	9	9	1G		
Gold				0.1	5% (J)	
Silver				0.01	10% (K)	
None					20% (M)	

### 12) Connecting of Resistors

Connecting resistors in series;  $R = R1 + R2 + R3 \dots$

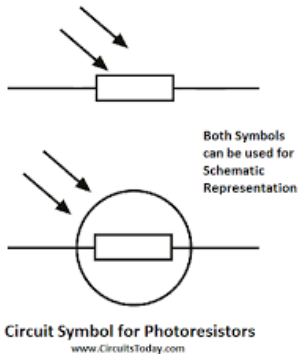
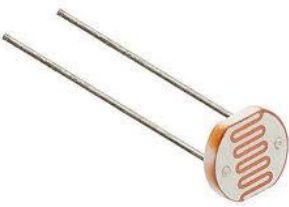
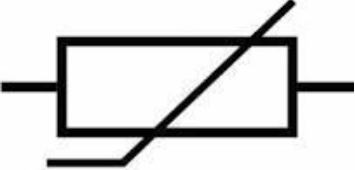

Connecting resistors in parallel;  $\frac{1}{R} = \frac{1}{R1} + \frac{1}{R2} + \frac{1}{R3} \dots$

### 13) Ohms Law


Ohm's Law is the relationship between voltage, current, and resistance.

Formula;  $V = IR$ , where  $V = \text{Voltage}$ ,  $I = \text{Current}$ , and  $R = \text{Resistance}$

### 14) Input Devices [Sensors]

Name	Schematic Representation	Pictorial Representation	Function of Component
Light Dependent Resistor (LDR)			Transducer converts brightness to resistance. Resistance of LDR changes w/ light intensity.
Thermistor			A thermal resistor that changes resistance w/ temperature. Converts temperature to resistance

### 15) Soldering

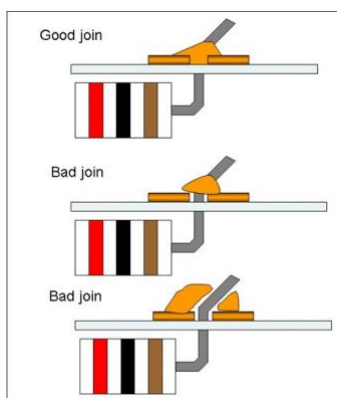


Component within Electronics	Relation with Physics by topic
4b – Battery, Potential Difference, EMF	Current of Electricity
5 – Electrical Current and Power, Formula $P=VI$	Current of Electricity, Practical Electricity
6 - Usage of ammeter and voltmeter	Current of Electricity
7- Circuits	DC Circuit
13 – Ohms Law, formula $V = I R$	Current of Electricity
12 – Connecting of Resistors	Current of Electricity

## COMMON ELECTRICAL SYMBOLS



connecting wire

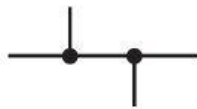


wires joined



wires crossing (no contact)



cell

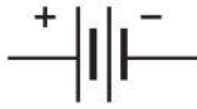

2 cells / battery



battery (with many cells)



direct current (DC)  
power supply



alternating current (AC)  
power supply



coil of wire / solenoid




galvanometer



ammeter



milliammeter

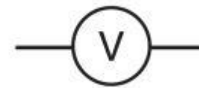

voltmeter




switch




two-way switch



bulb / filament bulb

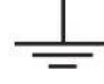


earth

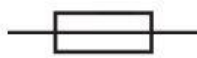

fuse



fixed resistor

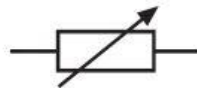

variable resistor



thermistor




light dependent  
resistor (LDR)



diode



light emitting  
diode (LED)

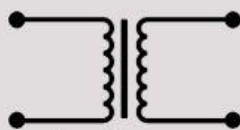

transformer



bell



buzzer

evan.toh



