

# Current Electricity



1 / 1



Add Source

Science

Secondary 4 Physics

- The direction of the flow of electrons is from the **negative** terminal to the **positive** terminal.
- The flow of electric current is in the direction opposite to that of the flow of electrons.
- Like electrons charges repel each other (for example, an electron has a negative charge and another electron has a negative charge, so they both will repel)
  - Likewise, opposing poles attract, just like a magnet
  -

## What is Electric Current?


An electric current is formed by **moving charges**.

An electric current is a measure of the **rate of flow** of electric charge through a given cross-section of a conductor.



where  $I$  = current;  
 $Q$  = charge;  
 $t$  = time taken.

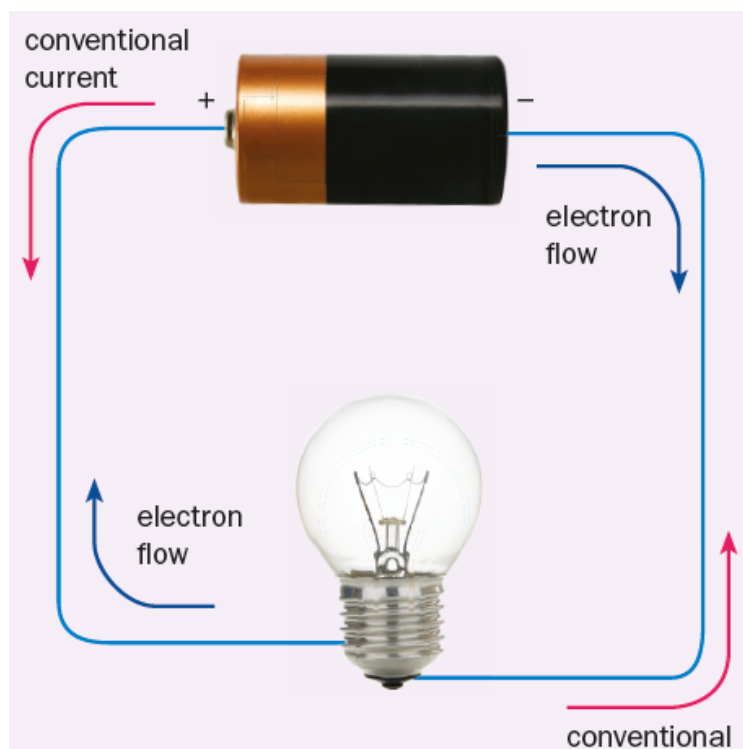The SI unit of electric current is the **ampere (A)**.



▶ [Flow of Electricity through a Circuit | Electricity and Circuits | Don't Memorise - YouTube](#)

- The negative terminal of the cell repels the electrons near it, and the electrons which get repelled go in the downwards direction
- Electron flow is from negative to positive end of the battery and direction of current is from positive to negative ends of the battery

The formula of electric current is  $I = Q/t$

Where,

- $I$  = Charge,  $Q$  = Current and  $t$  = time

The S.I Unit of Current is Ampere (A)

### **So, how did a conventional current get its name?**

Before the discovery of electrons, scientists believed that electric current was caused by the movement of positive charges.

Although this idea was later proven wrong, the idea remains.


This 'movement' of positive charges is called conventional current.

Electric current is actually caused by the flow of electrons from the negative terminal to the positive terminal.
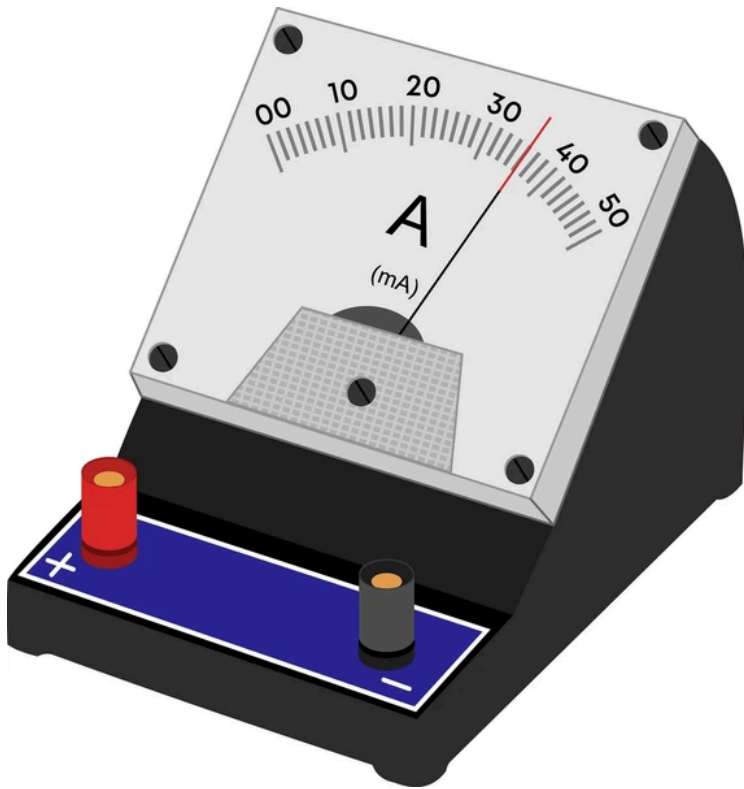
### **How do we measure currents?**


An ammeter is used to measure current

It should be connected in series to the circuit








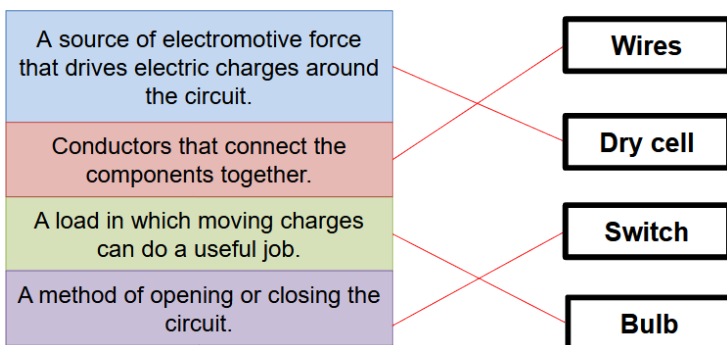

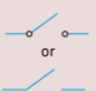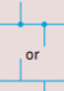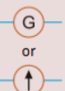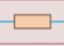

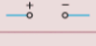
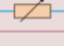







### Main Components of a Circuit

- A typical electric circuit consists of four main components.




## Drawing Circuit Diagrams


Some common components and their symbols are listed in the tables below.

Symbol	Device	Symbol	Device	Symbol	Device
	switch		wires joined		galvanometer
	cell		wires crossed		ammeter
	battery		fixed resistor		voltmeter
	d.c. power supply		variable resistor (rheostat)		two-way switch
	a.c. power supply		fuse		earth connector
	light bulb		coil of wire		capacitor

## Open and closed circuits

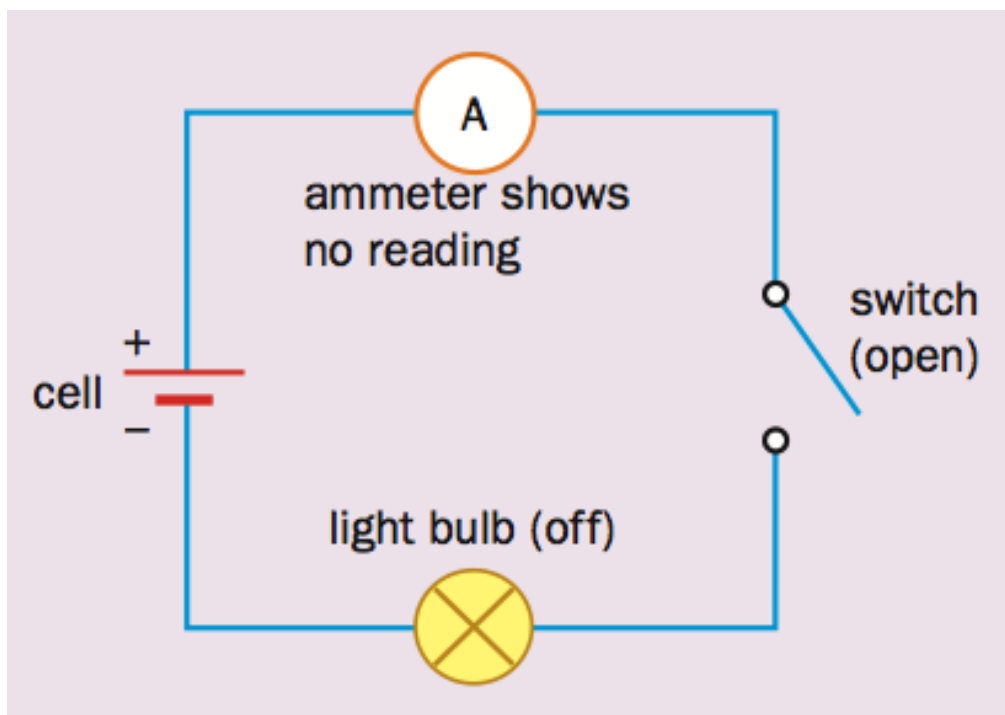

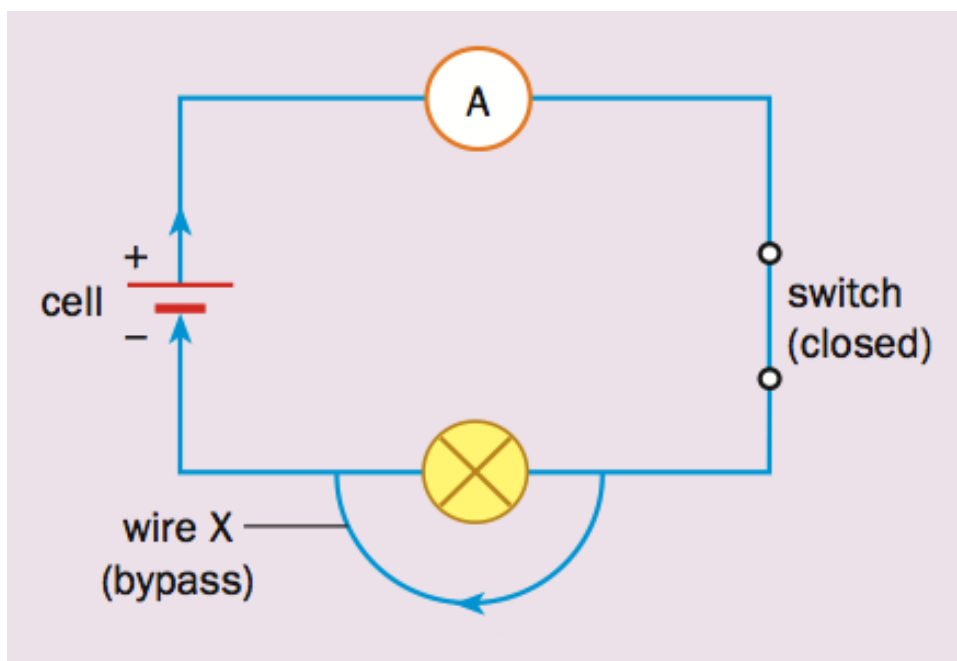An open circuit is a circuit in which current is unable to flow due to breaks in the circuit





A closed circuit allows electricity to flow through without any interruptions (but in this diagram, the bulb will not light up due to the least resistance being on the bypass)

### Electromotive Force and Potential Difference

## 17.2 Electromotive Force and Potential Difference

### What is Electromotive Force?

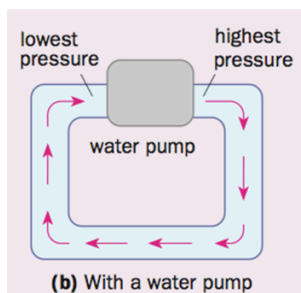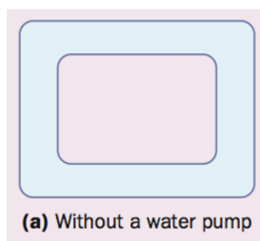

- A battery functions like a water pump.
- A water pump does work (providing energy) to drive the water around the pipe.
- The water pump does not supply the water in the pipe.
- Likewise, a battery does work to drive **electrons** around the circuit.

The **electromotive force** (e.m.f) of an electrical energy source is defined as the **work done by the source** in driving a **unit charge** around a **complete circuit**.

Formula

$$\varepsilon = \frac{W}{Q}$$

where  $\varepsilon$  = e.m.f. of electrical energy source;

$W$  = work done (amount of non-electrical energy converted to electrical energy);

$Q$  = amount of charge.

The SI unit of e.m.f is the **joule per coulomb ( $\text{J C}^{-1}$ )** or **volt (V)**.

So, e.m.f is basically volt!

**How do we measure e.m.f?**

We make use of a voltmeter to measure volt, which is the SI unit of e.m.f

**Series and Parallel arrangement**

- In series, e.m.f resultant is equal to  $e.m.f_1 + e.m.f_2 \dots$
- In parallel, e.m.f resultant is equal to  $e.m.f_1 = e.m.f_2 \dots$

### **Potential Difference**

What is the main difference between Potential difference and Electromotive Force?  
(underlined)

The **potential difference** (p.d.) across a component in an electric circuit is the **work done to drive a unit charge through the component.**

The **electromotive force** (e.m.f) of an electrical energy source is defined as the **work done by the source** in driving a **unit charge** around a complete circuit.

### **Formula**

where  $V$  = p.d. across a component;

$W$  = work done (amount of electrical energy converted to other forms);

$Q$  = amount of charge.

The SI unit of potential difference is the **volt (V)**.

\*Ammeter should be connected to the circuit in series and voltmeter is connected in parallel to the circuit



What is the answer to this question?

The answer

is A and C

### **Resistance**

The resistance of a component is the **ratio** of the **potential difference** across the component to the **current** flowing through the component.

The higher the resistance is, the more difficult it is for the current to flow.

### **Formula**

$$R = V/I$$

where R = resistance of a component;

V = p.d. across a component;

I = current flowing through component.

The SI unit of resistance is the **ohm** ( $\Omega$ ).

### **What are Resistors?**

- A resistor is a conductor in a circuit that is used to control the size of the current flowing in a circuit.
- There are two types of resistors — **fixed** resistors and **variable** resistors (or rheostats).

**Resistivity formula**

$$\rho = RA/l$$

where  $\rho$  = resistivity of conductor;

R = resistance of conductor;

A = cross-sectional area of conductor;

l = length of conductor.

The SI unit of resistivity is the **ohm metre ( $\Omega \text{ m}$ )**.

- **Resistivity** is a property of the material and it is **independent** of the dimensions of the material.

<div> <div>Current Electricity</div> <div> <div>Filter</div> <div>Sort</div> <div>Table ▼</div> </div> </div>		
Resistivity of Materials (N...	Material	Resistivity
	Silver	$1.6 \times 10^{-6}$
	Copper	$1.7 \times 10^{-8}$
	Tungsten	$5.5 \times 10^{-8}$
	Iron	$9.8 \times 10^{-8}$
	Constantan	$49 \times 10^{-8}$
	Nichrome	$100 \times 10^{-8}$
	Graphite	$3000 \times 10^{-8}$
	Polythylene	about $10^{16}$
+		

