

Tutorial 18

ALTERNATING CURRENTS



Self-Check Questions

- S1. What is meant by period, frequency, peak value and root-mean square current as applied to an alternating current?
- S2. A sinusoidal current is represented by the equation $I = I_o \sin(\omega t)$. What is its period, frequency, peak value and root-mean square value?
- S3. Deduce that the mean power in a resistive load is half the maximum power for a sinusoidal alternating current.
- S4. What is the relationship between r.m.s. and peak values for a sinusoidal current?
- S5. Explain the principle of operation of a simple iron-core transformer.
- S6. For an ideal transformer, what is the relationship between the turns ratio of windings, the input and output potential differences, and the primary and secondary currents?
- S7. Explain how a diode is used for rectification of an alternating current.

Self-Practice Questions

- SP1. (a) What is meant by the r.m.s. value of an alternating current?
- (b) Calculate the peak value of a 240 V mains electricity supply.
- (c) A sinusoidal alternating current of r.m.s. value 5.0 A passes through a 4.0Ω resistor. Calculate
- (i) the peak value of the current,
 - (ii) the mean power in the resistor,
 - (iii) the maximum power in the resistor.

SP2.



- (a) The figure above shows the variation with time t of a periodic current I . Determine
- (i) the average value of the current,
 - (ii) the root-mean-square current.
- (b) The periodic current passes through a resistor, producing heat at a certain rate. State the steady current, when passed through the same resistor, would have an identical heating effect.

(J83/I/10)

SP3. A mains electricity supply has a r.m.s. voltage of 240 V and a peak voltage of 340 V. When connected to this supply, a heater dissipates energy at a rate of 1000 W. The heater is then connected to a 340 V d.c. supply and its resistance remains the same. At what rate does the heater now dissipate energy? (N2000/I/21)

SP4. The primary coil of a transformer is connected to an alternating voltage supply. The secondary coil is connected across a variable resistor. Suggest ways in which you can decrease the p.d. across the secondary coil.


SP5. In a laboratory experiment to test a transformer, a student obtained the following results.

V_p / V	I_p / mA	N_p turns	V_s / V	I_s / mA	N_s turns
240	2.0	?	?	50	50

Assuming the transformer is 100% efficient, what are the missing entries?

(Modified from J93/I/20)

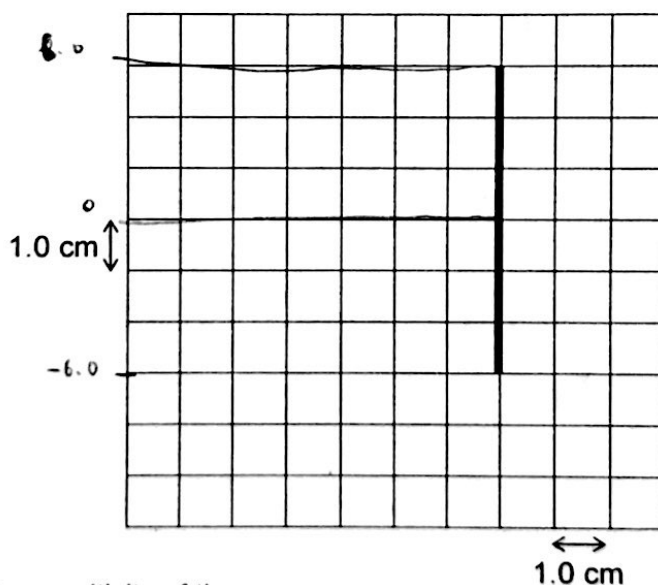SP6. The diagram shows the display on a cathode-ray oscilloscope (c.r.o.) when a sinusoidal p.d. is applied to the Y-input. The r.m.s. value of the applied p.d. is 4.24 V. The time-base is switched off.




Calculate the Y-plate sensitivity of the c.r.o.

Discussion Questions

Characteristics of Alternating Currents

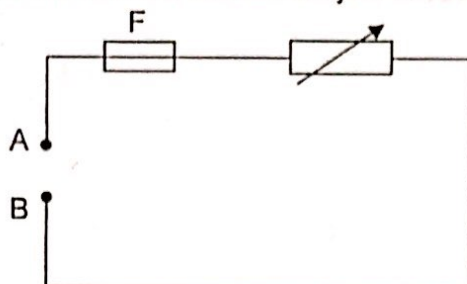- D1. When an a.c. supply of 240 V r.m.s. is connected to the terminals AB in the circuit shown below, the fuse F breaks the circuit if the current just exceeds 13 A r.m.s.



When the a.c. supply is replaced with a 120 V d.c. source, an identical fuse breaks the circuit if the current just exceeds

A $\frac{13}{2}$ A

B $\frac{13}{\sqrt{2}}$ A

C

(J88/II/23)

- D2. A sinusoidal potential V_1 shown in Fig. 2a is applied across a resistor R which produces heat at a mean rate P .

Determine the mean rate of heat production when the square-wave of potential V_2 shown in Fig. 2b is applied across the same resistor.

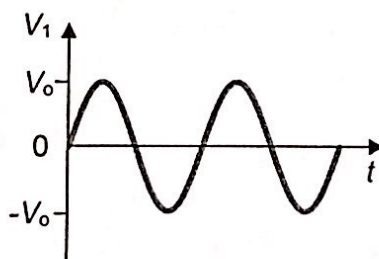


Fig. 2a

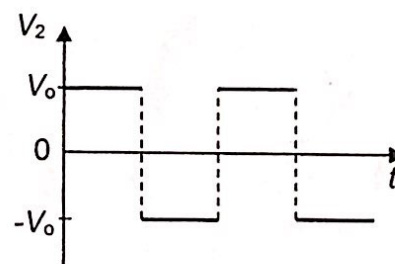



Fig. 2b

(J82/II/18)


[2]

- D3. (a) Calculate the r.m.s. current of (i) and (ii).

[2]

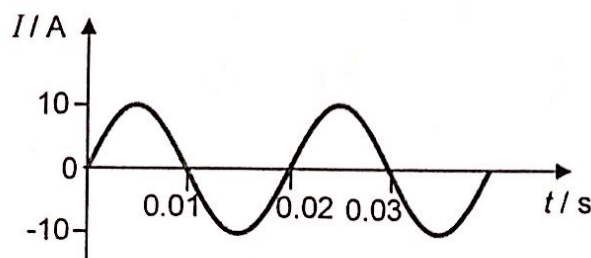

(i)

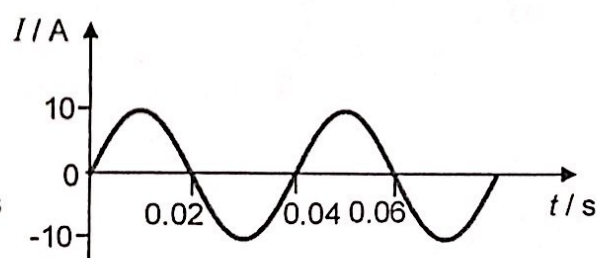



(ii)

- (b) What can you conclude from your answers to (i) and (ii)?


[1]

(c) Determine the r.m.s. current of (iii) and (iv).

[4]

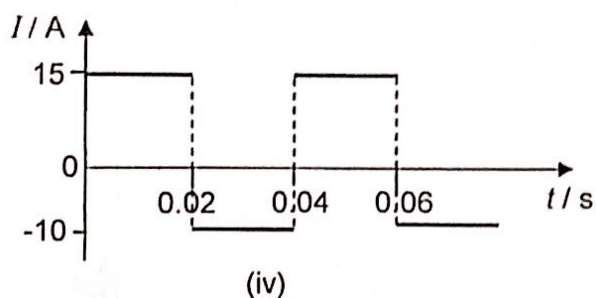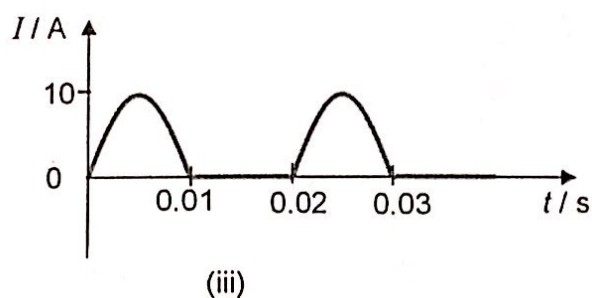

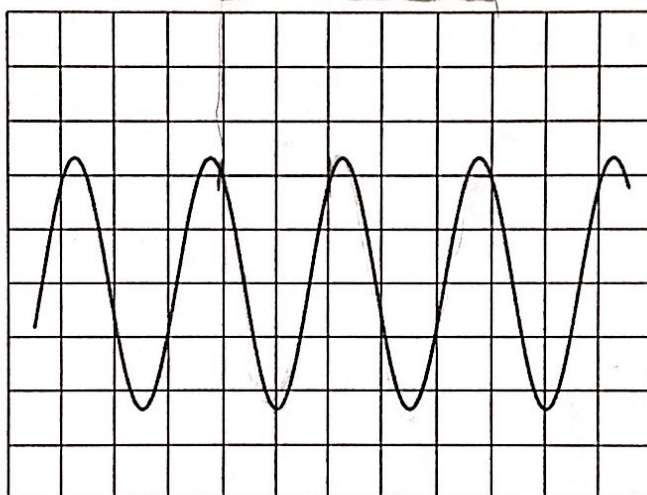- D4. A cathode-ray oscilloscope (c.r.o.) is connected across the output of a transformer and the screen is as shown below. The squares on the screen have sides of one centimetre.




The Y-plate sensitivity is set at 2.0 V cm^{-1} and the timebase is set so that the horizontal deflection is 0.50 ms cm^{-1} .

For the alternating potential difference applied to the Y-plates, deduce the values of the following quantities:

- | | |
|---|-----|
| (a) period, | [1] |
| (b) frequency, | [1] |
| (c) peak value of potential difference, | [1] |
| (d) root-mean-square value of potential difference. | [1] |



Rectification

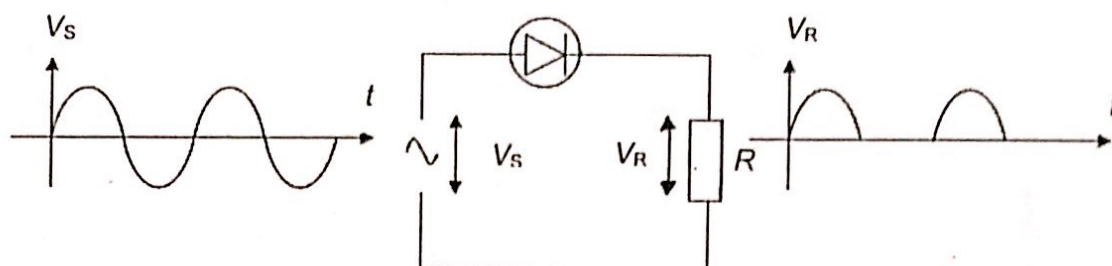- D7. An alternating supply is applied to a resistor R with a diode connected in series with it. The time t variation of the supply voltage V_S and the p.d. V_R across the resistor are shown in the diagram.








Which of the following statements is *incorrect*?

- A Half-wave rectification takes place so that the current supplied to the resistor is one-directional.
 - B The period of the V_R - t graph is half of that of the V_S - t graph.
 - C The time intervals corresponding to zero voltage across resistor R in the graph represent the stages when the diode is reverse-biased.
 - D Root-mean-square voltage across resistor R is half of the peak voltage applied across it.
- D8. The circuit represents a bridge rectifier arrangement. The graph below shows the variation over one cycle of the potential of X with respect to Y .

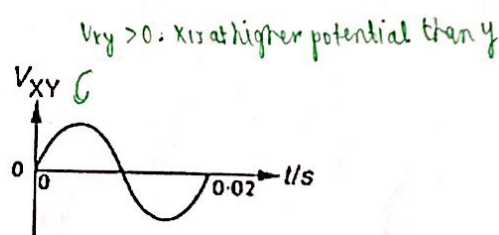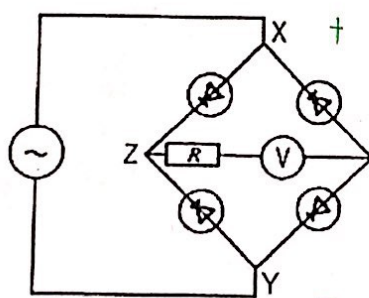


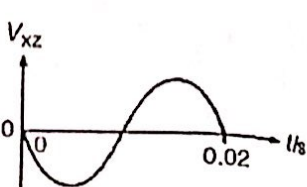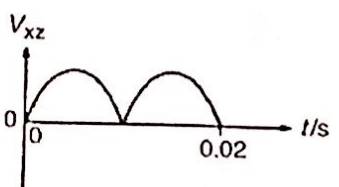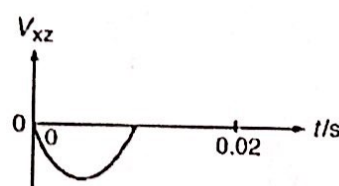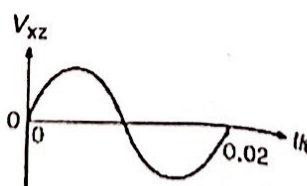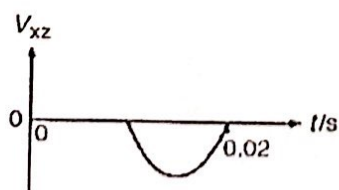Which one of the graphs best represents the corresponding variation of the potential of X with respect to Z ?



The transformer

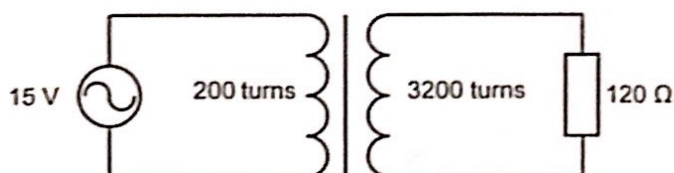- D5. The primary of an ideal transformer has 200 turns and is connected to a 15 V supply. The secondary has 3200 turns and is connected to a resistor of resistance $120\ \Omega$, as shown in the diagram.




What are possible values of the secondary voltage, the secondary current and the mean power dissipated in the resistor?

	secondary voltage / V r.m.s.	secondary current / A r.m.s.	resistor power / W
A	24	0.020	4.8
B	24	0.20	48
C	240	0.50	120
D	240	2.0	480

(N2011/1/33)

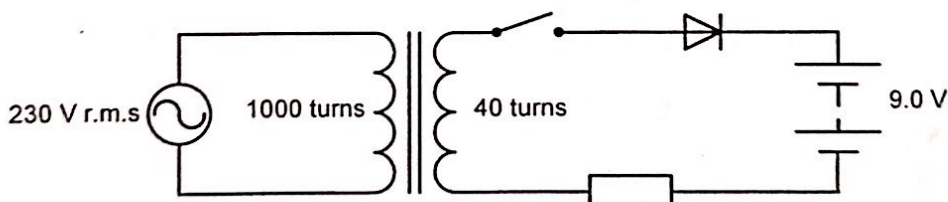- D6. The primary coil of a transformer has 1000 turns and is connected to a 230 V r.m.s. supply. The secondary coil has 40 turns and may be connected, through a switch and a diode, to a 9.0 V rechargeable battery, as illustrated in the figure below.



- (a) Initially the switch is open. Considering both the transformer and the diode to be ideal, calculate
- the r.m.s. potential difference across the secondary, [1]
 - the peak potential difference across the secondary. [1]
- (b) The switch is now closed so that the battery is being recharged.
- Suggest why the diode is necessary in the secondary circuit. [1]
 - Suggest why the resistor is necessary in the circuit. [1]

(J2000/II/5)

Challenging Questions

- C1. Two air-core solenoids P and Q which are identical in length and area of cross-section, have 10 and 50 turns respectively. They are placed near each other.

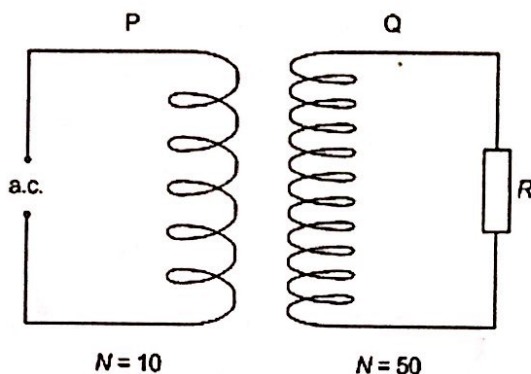


Fig 23.1

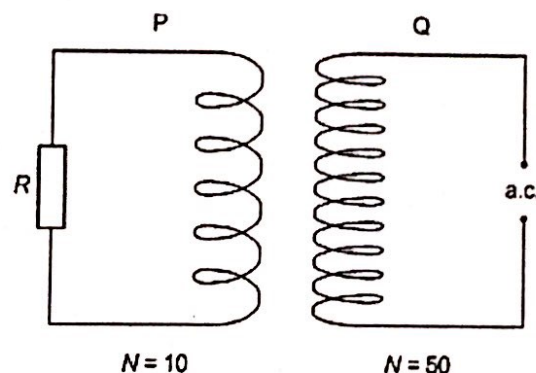


Fig 23.2


In Fig. 23.1, when the current in P changes at a rate of 5.0 A s^{-1} , an e.m.f. of 2.0 mV is induced in Q. The current in P is then switched off. In Fig. 23.2, a current which is changing at 2.0 A s^{-1} is then sent through Q. What e.m.f. will be induced in P?

[Magnetic flux density in a solenoid, $B = \mu_0 n I$ where μ_0 is the permeability of free space, n is the number of turns per unit length and I is the current in the solenoid.]

*Knowledge of mutual inductance is required in this question.

(RJC 2004 Prelim P1 Q23)

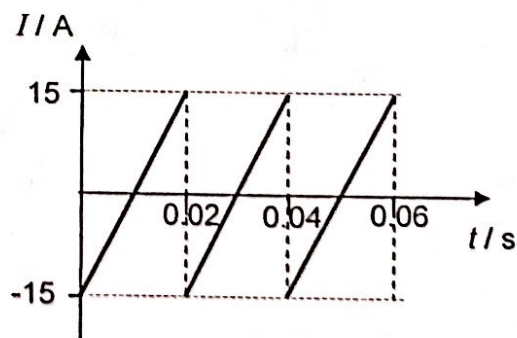- C2. Determine the r.m.s. current shown in the figure.



- Ans:
- SP1. 339 V, 7.07 A, 100 W, 200 W
 - SP2. 1.0 A, 2.0 A, 2.0 A
 - SP3. 2000 W
 - SP5. 1250, 9.6 V
 - SP6. 2.0 V cm^{-1}
 - D1. C
 - D2. $2P$
 - D3. 7.07 A, 5.00 A, 12.7 A
 - D4. 1.25 ms, 800 Hz, 4.7 V, 3.3 V
 - D5. D
 - D6. 9.2 V, 13.0 V
 - D7. B
 - D8. A
 - C1. $8.0 \times 10^{-4} \text{ V}$
 - C2. 8.66 A

TUTORIAL 18 SUGGESTED SOLUTIONS

SELF-CHECK QUESTIONS:

S1.	Term	Definition
	Period, T	of an alternating current is the time taken for one complete cycle.
	Frequency, f	of an alternating current is the number of complete cycles per unit time.
	Peak current, I_0	of an alternating current is the amplitude of the current.
	Root-mean square current, $I_{\text{r.m.s.}}$	of the alternating current is that value of direct current that would produce thermal energy at the same rate in a resistor.

S2. Period $T = \frac{2\pi}{\omega}$

Frequency $f = \frac{1}{T} = \frac{\omega}{2\pi}$

Peak value is I_0

Root-mean square value $I_{\text{r.m.s.}} = \frac{I_0}{\sqrt{2}}$

S3. The instantaneous power delivered to R at time t is

$$P = IV_R = (I_0 \sin \omega t)(V_0 \sin \omega t) = I_0 V_0 \sin^2 \omega t$$

The mean power is given by

$$\langle P \rangle = \langle I_0 V_0 \sin^2 \omega t \rangle = I_0 V_0 \langle \sin^2 \omega t \rangle = I_0 V_0 \left(\frac{1}{2} \right) = \frac{P_0}{2}$$

i.e. mean power in a resistive load is half the maximum power for a sinusoidal a.c.

*Proof for yourself that $\langle \sin^2 \omega t \rangle = \frac{1}{2}$

S4. $I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$



S5. The principle of operation of a simple iron-core transformer:

- a transformer works by electromagnetic induction
- the a.c. source causes an alternating current to flow in the primary coil, which sets up an alternating magnetic flux in the iron core
- this induces an alternating e.m.f. in the secondary coil, in accordance with Faraday's law of electromagnetic induction
- the induced e.m.f. in the secondary coil give rise to an alternating current which delivers energy to the device to which the secondary is connected
- all currents and e.m.f.s have the same frequency as the a.c. source

S6. For an ideal transformer:

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$$

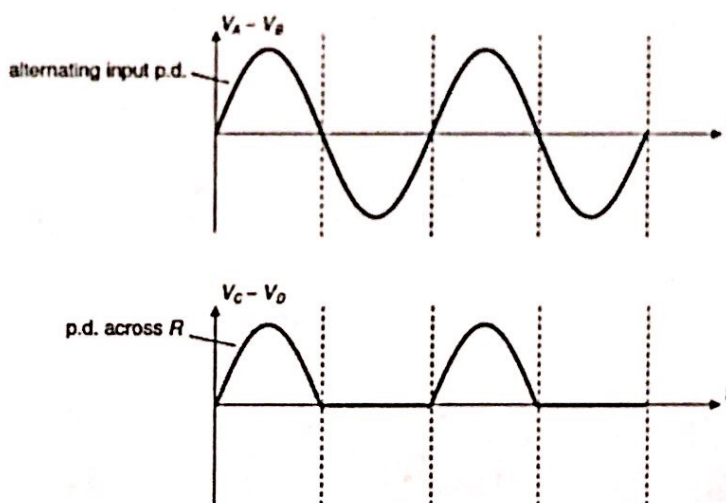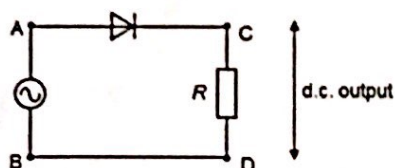
- S7. 1. Connect a diode in circuit as shown below.
 2. Diode allows current to flow during one-half of a cycle when it is forward biased.
 3. When it is reverse bias, no current flows through R .



SELF-PRACTICE QUESTIONS:

- SP1. (a) The r.m.s. value of the alternating current is the value of the direct current that would produce thermal energy at the same rate in a resistor.
- (b) For a 240 V mains electricity supply, $V_{\text{rms}} = 240 \text{ V}$.
 The peak value of the 240 V mains, $V_0 = \sqrt{2} V_{\text{rms}} = \sqrt{2} (240 \text{ V}) = 339 \text{ V}$.
- (c) A sinusoidal alternating current of r.m.s. value 5.0 A passes through a 4.0Ω resistor.
- Peak value of the current $I_0 = \sqrt{2} I_{\text{rms}} = \sqrt{2} (5.0 \text{ A}) = 7.07 \text{ A}$
 - Mean power in the resistor $\langle P \rangle = I_{\text{rms}}^2 R = 5.0^2 \times 4.0 = 100 \text{ W}$
 - Maximum power $P_0 = 2 \langle P \rangle = 2 \times 100 = 200 \text{ W}$

SP2.

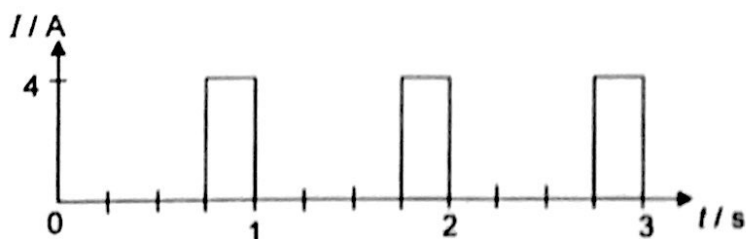

(a)(i) Average value of the current = $\frac{0 \times 0.75 + 4 \times 0.25}{1} = 1.0 \text{ A}$

(ii) Root-mean-square current = $\sqrt{\frac{0 \times 0.75 + 4^2 \times 0.25}{1}} = 2.0 \text{ A}$

(b) A steady current of 2.0 A will produce an identical heating effect as the alternating current. This is according to the definition of r.m.s. value of an alternating current.

SP3.

$$\langle P \rangle = \frac{V_{\text{rms}}^2}{R} \Rightarrow R = \frac{V_{\text{rms}}^2}{\langle P \rangle} = \frac{240^2}{1000}$$

Power dissipated in 340 V d.c. source = $\frac{V_{\text{d.c.}}^2}{R} = \frac{340^2}{\left(\frac{240^2}{1000}\right)} = 2000 \text{ W}$

OR we can treat 340 V d.c. as V_0 , then $P_0 = 2\langle P \rangle = 2000 \text{ W}$

SP4.

Since $\frac{V_s}{V_p} = \frac{N_s}{N_p}$, to decrease the p.d. V_s across the secondary coil, we can

- increase N_p , the number of turns in the primary coil
- decrease N_s , the number of turns in the secondary coil
- decrease V_p , the supply voltage that is connected to the primary coil


*changing the resistance of the variable resistor will not affect the p.d. across the secondary coil.

SP5.

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = \frac{I_p}{I_s} = \frac{2.0}{50}$$

$$N_p = \frac{50}{2.0} \times N_s = \frac{50}{2.0} \times 50 = 1250$$

$$V_s = \frac{2.0}{50} \times V_p = \frac{2.0}{50} \times 240 = 9.6 \text{ V}$$

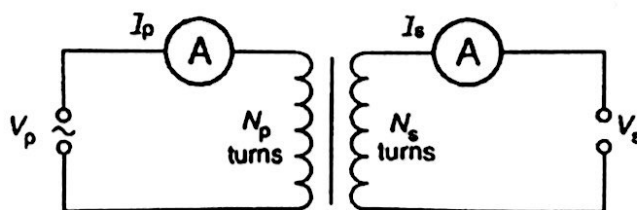

SP6.

For sinusoidal p.d.,

$$V_0 = \sqrt{2} V_{\text{r.m.s.}} = \sqrt{2} (4.24 \text{ V}) = 6.0 \text{ V}$$

From the diagram,

peak-to-peak p.d. has a span of 6.0 cm

$\Rightarrow V_0$ has a span of 3.0 cm

$\Rightarrow 6.0 \text{ V}$ has a span of 3.0 cm

$$\therefore \text{Y-plate sensitivity} = \frac{6.0 \text{ V}}{3.0 \text{ cm}} = 2.0 \text{ V cm}^{-1}$$