# Chapter 18 ALTERNATING CURRENT

## Content

- Characteristics of alternating currents
- The transformer
- Rectification with a diode

# Learning Outcomes

Candidates should be able to

(a)	show an understanding of and use the terms period, frequency, peak		
	value and root-mean-square (r.m.s.) value as applied to an alternating		
	current or voltage.		
(b)	deduce that the mean power in a resistive load is half the maximum		
	(peak) power for a sinusoidal alternating current.		
(c)	represent an alternating current or an alternating voltage by an		
	equation in the from $x = x_0 \sin \omega t$		
(d)	distinguish between r.m.s. and peak values and recall and solve		
	problems using the relationship $I_{rms} = \frac{I_o}{\sqrt{2}}$ for the sinusoidal case.		
(e)	show an understanding of the principle of operation of a simple iron-		
	cored transformer and recall and solve problems using $\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$		
	for an ideal transformer.		
(f)	explain the use of a single diode for the half-wave rectification of an		

alternating current.

## 18.1 Introduction

An alternating current (a.c.) is an electric current which has a flow direction that reverses periodically with time. An a.c. at the microscopic level can be considered as having the charge carriers oscillate about a fixed point.



Examples of Alternating Current (a.c.)

It is important to understand a.c. because they are so much a part of our everyday life. Each time a television set, computer or any other electric appliances which are connected to the wall socket are turned on, an a.c. provides the power to operate them. The principles of direct current in resistors learned in previous topics can be applied to resistors in a.c. circuits. However, major differences in circuit analysis arise when inductors and capacitors are to be considered.

Quantity	Symbol	Description
Period	Т	The time taken for the a.c. to complete one cycle.
Frequency	f	The number of complete cycles undergone by the a.c. in one second.
Angular	ω	A way of expressing the frequency of the a.c. in terms of radians
Frequency		per second instead of cycles per second.
Peak Value	Io	The maximum value of the a.c. in either direction within a cycle.
(Amplitude)		
Peak to Peak		The difference between the positive peak value and the negative
Value		peak value of the a.c. within a cycle.
Mean Value	< <i>I</i> >	The average value of an a.c. over a given time interval.
Root Mean	Irms	The value of a steady d.c. that will dissipate energy at the same
Square Value		rate as the a.c. in a given resistor.

## **18.2** Quantities Characterising an Alternating Current

## 18.3 Sinusoidal Alternating Current

The most commonly encountered a.c. takes a sinusoidal form as shown and the waveform can be expressed by the equation

$$I = I_o sin\omega t$$

As voltage is related to current by the equation V = IR,

$$V = (I_0 \sin \omega t)R$$
$$= (I_0 R) \sin \omega t$$
$$= V_0 \sin \omega t$$

Hence, current and voltage across a resistor are in phase.



For any positive value of current, there will be a corresponding negative value within a complete cycle, thus the mean value of current  $\langle I \rangle$  is zero. However heat is dissipated when an a.c. flows in a resistor, effectively implying that the mean value of an a.c. does not represent the effective value of the a.c.

## 18.4 Mean Power

The instantaneous power, *P*, is given by the following equations,

$$P = IV \qquad P = I^{2}R \qquad P = I^{2}R \qquad P = \frac{V^{2}}{R} \qquad P = \frac{V^{2}$$

Graphically,



The mean power,  $\langle P \rangle$ , can be found by considering the graph of P - t,



Notice that the shaded regions under the curve and above the dashed line (A) have the same area as the shaded regions above the curve and below the dashed line (B). Thus, the mean power in a resistive load is **half** the maximum power for a **sinusoidal alternating current** i.e.

$$\langle P \rangle = \frac{P_0}{2}$$

Note:

- 1. The period of power is half that of the sinusoidal a.c. and therefore its frequency is twice the frequency of a.c.
- 2. Mean power is half the maximum power i.e.  $\langle P \rangle = \frac{P_0}{2}$ , for sinusoidal a.c. only.

## 18.5 Root Mean Square Value



Since energy is dissipated at the same rate then  $I_{dc} = I_{rms.}$ 

 $I_{rms}$  is the square root of the mean value of  $I^2$  and hence is known as the root-mean-square (r.m.s.) current of the a.c.

The r.m.s. value of an a.c. is the value of a steady d.c. which will dissipate energy at the same rate as the mean power dissipated by an a.c. in a given resistor.

Thus the r.m.s. value can be considered as the effective value of the a.c.

## 18.5.1 Root Mean Square Value (Graphical)

As the area under a P - t graph would yield the energy dissipated in the given resistor, the area under the  $P_{instantaneous}$  - t graph must be equal to the area under the  $P_{mean}$  - t graph such that the energy dissipated is the same.

For a sinusoidal alternating current



\* Mathematically, it can be shown that Shaded Area A = Shaded Area B

From the above graphs, it can be seen that *for a sinusoidal alternating current*,

$$\langle P \rangle = \left(\frac{I_o^2}{2}\right)R = I_{rms}^2 R$$
$$I_{rms}^2 = \frac{I_o^2}{2}$$
$$I_{rms} = \frac{I_o}{\sqrt{2}}$$

Hence <u>for a sinusoidal alternating current</u>, the r.m.s. value of the current  $I_{rms}$  is related to the peak current  $I_o$  by the expression

$$I_{rms} = \frac{I_o}{\sqrt{2}}$$

Similarly,

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

## General Knowledge

The alternating electrical supply from wall sockets in Singapore is 240 V, 50 Hz. Is 240 V the peak value, or the r.m.s. value of the supply?

	٩.	٠	
. 4.	1		*
	5		1
			2

#### Problem Solving Skill Set (PS<sup>3</sup>)

- 1. Consider one period of the alternating quantity.
- 2. Square the quantity.
- 3. Mean (average) the squared quantity.
- 4. Square root the mean-square quantity.

Since r.m.s. values are the effective values of a.c.,

$$\langle P \rangle = I_{ms} V_{ms}$$
 or  $\langle P \rangle = I_{ms}^2 R$  or  $\langle P \rangle = \frac{V_{ms}}{R}$ 

## For a sinusoidal a.c.,

$$\langle P \rangle = I_{rms} V_{rms}$$

$$= \left(\frac{I_0}{\sqrt{2}}\right) \left(\frac{V_0}{\sqrt{2}}\right)$$

$$= \frac{I_0 V_0}{2}$$

$$= \frac{P_0}{2}$$

which is the same result as shown previously.

Note:

- 1. The expressions  $I_{rms} = \frac{I_0}{\sqrt{2}}$  and  $V_{rms} = \frac{V_0}{\sqrt{2}}$  are only true for sinusoidal a.c.
- 2. The three equations for mean power i.e.  $\langle P \rangle = I_{rms}V_{rms}$ ,  $\langle P \rangle = I_{rms}^2 R$  and  $\langle P \rangle = \frac{V_{rms}^2}{R}$  can be used for all types of a.c.
- 3. Current and voltage ratings in electrical appliances/supplies are expressed in r.m.s. values.
- 4. Power ratings in electrical appliances/supplies refer to the mean (average) power.



# Example 2

A tourist from U.S.A. brings an electric water kettle designed to operate with 110 V to Singapore and plugs it into a 240 V outlet. The heater breaks down due to overheating.

(a) If the heater normally consumes 500 W, calculate the resistance of the heating coil.

$$\langle P \rangle = \frac{V_{rms}^2}{R}$$
$$500 = \frac{110^2}{R}$$
$$R = 24.2 \Omega$$

(b) Determine the power it consume using our 240 V electrical supply.

#### Assuming that *R* remains constant

 $\langle P \rangle = \frac{V_{rms}^2}{R}$  $= \frac{240^2}{24.2}$ = 2380 W

(c) Determine the r.m.s. current that flows when the potential difference is 240 V.

$$I_{rms} = \frac{V_{rms}^2}{R} = \frac{240}{24.2} = 9.9 \text{ A}$$

## 18.6 The Transformer

The transformer is a device that is used for increasing (stepping up) or decreasing (stepping down) the potential difference (p.d.) of an alternating supply using electromagnetic induction and it plays an important role in the transmission of electricity. Power plants are often situated some distance from the city and electricity must be transmitted over long distances to reach the consumers. Inevitably, some power is lost in the transmission lines. This power loss can be minimized if the power is transmitted at high p.d. (and consequentially, low current).



Two insulated copper coils, called the primary and secondary coils, not electrically connected to one another, are wound on separate limbs of a soft iron core, which is laminated to reduce eddy current losses. The soft iron core ensures that most of the flux associated with one coil also passes through the other. When an alternating voltage is applied to the primary coil, the resulting current produces a large alternating magnetic flux which links the secondary coil and induces an e.m.f. in it.

## 18.7 The Ideal Transformer

An ideal transformer is one in which there is <u>no energy loss</u> when stepping up or down the primary e.m.f.

$$\frac{N_s}{N_p} = \frac{V_s}{V_p}$$

where,

 $N_p$  = no. of turns in the primary coil,

 $N_s$  = no. of turns in the secondary coil,

 $V_{\rho}$  = e.m.f. in the primary coil,

 $V_s$  = e.m.f. in the secondary coil

\* It should be noted that the output waveform in the secondary coil is  $\pi$  rad out of phase with the input waveform to the primary coil.

Also for an ideal transformer, the power input at the primary coil is equal to the power output at the secondary circuit. Hence:

$$I_p V_p = I_s V_s$$
$$\frac{V_s}{V_p} = \frac{I_p}{I_s}$$

Thus for an ideal transformer:

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$$

## 18.8 The Practical Transformer

Practical transformers lose power through

(i) Resistance of the windings (coils):

The wires used for the windings of the coils have resistance and so heating occurs, resulting in power loss ( $l^2 R$ ). This form of power loss is also known as Joule heating. Thicker wires made of material with low resistivity (i.e. high purity copper) are used to reduce this power loss.

(ii) Eddy Currents:

The alternating magnetic flux induces eddy currents in the iron core and cause heating. This effect is reduced by laminating the iron core. Laminations reduce the area of circuits in the core, and thus reduce the e.m.f. induced and current flowing within the core, which leads to a reduction in the energy lost.



(iii) Hysteresis:

There are hysteresis losses in the core. The magnetization of the core is repeatedly reversed by the alternating magnetic field. The energy required to magnetise the core (while the current is increasing) is not entirely recovered during demagnetisation. The difference in energy is lost as heat in the core. The energy loss is kept to a minimum by using a magnetic material with low hysteresis loss.



(iv) Flux Leakage:

The flux due to the primary may not all link to the secondary coil if the coil is badly designed or has air gaps in it. When flux is "leaked "to the surrounding, power is loss and thus not all the power from the primary coil can be transferred to the secondary coil.

Example 3

10 lamps rated 24 W, 12 V are connected in parallel with the mains supply of 240  $\,$ 

V.

(a) Calculate the turns ratio of the transformer needed.

Turns ratio:  $\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{12}{240} = \frac{1}{20}$ 

(b) Calculate the current drawn from the mains supply if the transformer is 100% efficient.

Current in each lamp,  $I_{rms} = \frac{\langle P \rangle}{V_{rms}} = \frac{24}{12} = 2.0 \text{ A}$ 

Since the lamps are connected in parallel, total current drawn in the secondary coil = 20 A.

Since transformer is assumed to be 100 % efficient,

 $I_P V_P = I_s V_s$ 240 $I_P = 12(20)$  $I_P = 1.0 \text{ A}$ 

(c) Determine the current drawn from the mains supply if the transformer is 91% efficient.

 $0.91I_PV_P = I_SV_S$   $0.91(240)I_P = 12(20)$  $I_P = 1.1 \text{ A}$ 

## Example 4

An average of 120 kW of electric power is sent to a small town from a power plant 10 km away. The transmission lines have a total resistance of 0.40  $\Omega$ . Calculate the power loss if the power is transmitted at (a) 240 V (b) 24 000 V.

 $\langle \boldsymbol{P} \rangle = \boldsymbol{I}_{rms} \boldsymbol{V}_{rms}$ 

- (a) At 240 V,  $I_{rms} = \frac{\langle P \rangle}{V_{rms}} = \frac{120 \times 10^3}{240} = 500 \text{ A}$ Power loss in the lines  $\langle P \rangle = I_{rms}^2 R_{cable} = 500^2 (0.4) = 1.0 \times 10^5 \text{ W}$
- (b) At 24 000 V,  $I_{rms} = \frac{\langle P \rangle}{V_{rms}} = \frac{120 \times 10^3}{24000} = 5 \text{ A}$ Power loss in the lines  $\langle P \rangle = I_{rms}^2 R_{cable} = 5^2(0, 4) = 10 \text{ W}$

### 18.9 Rectification

The e.m.f. obtained from the mains supply is alternating in nature, but we often require constant voltage to operate the electronic circuitries of many household devices. A means of deriving d.c. from a.c. is desired.

The process of converting a.c. to d.c. is known as rectification. This is achieved through the use of rectifiers which conduct current in one direction only. An example of a rectifier is the p-n diode which will be covered in the topic on lasers and semiconductors.

## 18.9.1 Half Wave Rectification

A diode is forward-biased when it is connected to a supply in such a way that current flows through it. It is reverse-biased if connected such that little or no current flows through it.



Forward-biased – current flows



Reverse-biased - negligible current flow

The a.c. to be rectified is connected in series with the diode and the electronic equipment that requires a d.c. output (represented by resistor R) as shown below.



Let us consider the case of a sinusoidal a.c. If the first half cycle acts in the forward-biased direction of the diode (i), current flows in the circuit and a p.d., V is obtained across R (which will have almost the same value as the applied p.d., V<sub>p</sub>, due to the low resistance of the diode when it is forward-biased). During the second half cycle, the diode is reverse-biased (ii). No current flows in the circuit and the p.d. across R is zero. This is repeated for each cycle of the a.c.



Hence, the output p.d. across *R* is a pulsating d.c.



#### APPENDIX A: FULL-WAVE RECTIFICATION

Source: http://www.circuitstoday.com/full-wave-bridge-rectifier

While a.c. is particularly important and useful in power generation and distribution, most electrical devices operate on d.c. sources only. Hence rectification of the a.c. is necessary. This can be done by using appropriate rectifiers and associated smoothing elements. The example below shows how a full-wave rectification could be introduced by using a full-wave (or bridge) rectifier. The circuit and output voltage for this layout is illustrated below.



During the positive half of cycle of the input voltage (i.e. when A is positive with respect to F), only diodes  $D_2$  and  $D_4$  are in forward bias and hence conduct. During the negative half of cycle of the input voltage (i.e. when F is positive with respect to A), only diodes  $D_3$  and  $D_1$  conduct. Since the current through the load *R* is unidirectional from C to D, the output voltage  $V_R$  is always positive. In this way, both halves of the a.c. voltage are rectified and we have a full-wave rectified voltage across *R*.

#### Full Wave Bridge Rectifier with Capacitor Filter

You can observe from the output diagram above that output of full-wave rectifier is not a constant d.c. voltage as it is a pulsating d.c. voltage with ac ripples. In real life applications,

we need a power supply with smooth wave forms as it directly impacts the reliability of the electronic device we connect to the power supply.

A simple way to do this is to large include а output reservoir capacitor in parallel to R. A capacitor is a conducting device capable of storing charges. It is made up of a pair of metal plates separated by an The action insulator. of capacitor in the full-wave rectifier will help to reduce the ripples and give a steadier output.



Resultant Output Waveform

#### **APPENDIX B: WIRELESS POWER CHARGING**

Source: http://www.explainthatstuff.com/inductionchargers.html

If you've got an electric toothbrush with a plastic bottom, you might have marveled at how it charges up apparently by magic standing on what seems to be a plastic stand! How do two bits of plastic charge up the battery inside your toothbrush when there is no direct metallic contact between them? How on Earth can electricity flow between two plastic insulators?

What's happening here is a neat trick called wireless (induction) charging, and it's the power behind everything from rechargeable toothbrushes and phone charging mats to the latest wireless recharging bays for electric cars. All these are based on the simple working mechanism of transformer.



#### How ordinary chargers work

Most of the small electronic appliances we use in our homes work on relatively low voltages—typically 5–10 percent as much voltage as hefty electric appliances like vacuum cleaners and clothes washers. That means we generally need to use transformers to "step down" the domestic voltage so it will safely power electronic gadgets without blowing them up. All those chargers actually have electricity transformers hiding inside.

charger:



#### How induction chargers work

It is just another kind of transformer in a cunning disguise. An electric toothbrush and its charger use a transformer that is cleverly split into two pieces.

When the toothbrush is standing on the peg, you've got a complete transformer that works by electromagnetic induction: magnetic flux from the primary coil in the charger unit is linked to the secondary coil in the toothbrush itself via the Ushaped iron core. The two ends of the coil in the toothbrush are simply hooked up to the rechargeable battery inside, allowing the latter to be charged.



outlet on your wall. Inside the charger, a

transformer "steps down" the electricity to a much lower voltage. The low-voltage current then flows from the charger into the battery in your appliance. The important thing to note is that all three parts of the transformer (the primary coil, secondary coil, and iron core linking them together) are contained inside the

A charger that works like this is called an induction charger. Safety is the main reason for using an induction charger in the bathroom: you don't need a power cable or exposed leads coming out of the base of your toothbrush, which typically gets wet. Electric shavers often use induction chargers for the same reason.

Find out more about the latest development in wireless chargers:

https://www.computerworld.com/article/3235176/mobile-wireless/wireless-charging-explained-what-is-it-and-how-does-it-work.html