D.C. Circuits

Resistors in Series

$$\mathbf{R}_{\text{total}} = \mathbf{R}_1 + \mathbf{R}_2 + \mathbf{R}_3$$

Resistors in Parallel

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Potential Divider Principle



Light Dependent Resistor (LDR)

A LDR is a resistor whose resistance <u>decreases</u> as light intensity falling on it <u>increases</u>. (Light falling on the LDR releases more charge carriers to conduct current.)

A thermistor (or thermally sensitive resistor) is a resistor whose resistance R_t changes greatly with <u>temperature</u>.

Thermistor

Commonly used thermistors have a *negative* temperature coefficient, i.e. resistance Rt <u>decreases</u> as temperature <u>increases</u>.

Electromotive force (e.m.f.), *E*, is the <u>amount of energy transferred per unit charge from some</u> <u>other form of energy into electrical energy</u> when charge is moved round a <u>complete circuit</u>.

$$\mathbf{E} = \frac{W}{Q}$$

Internal Resistance and Terminal potential diference

As shown in the diagram below, internal resistance is normally denoted as r and in a circuit it is denoted as a resistor that is in series with the source, and directly connected to the negative terminal. R is normally the external resistance (the load that is connected to the source, which is indicated by the dotted line circle.) While E is the e.m.f. of the source.



e.m.f. = p.d. across internal resistor + p.d. across external resistor

E = v + V

$$E = Ir + IR$$

IR = E - Ir

The quantity of (E - Ir) therefore indicates the amount of voltage that reaches the external components of a circuit and is known as the **terminal p.d.**

Perspective of power

Power generated by source = Sum of power dissipated in other components.

Hence, in the similar circuit,



$$P_{source} = p + P$$

$$IE = Iv + IV = I^2r + I^2R$$

where: p is the power dissipated due to internal resistance and P is the power dissipated due to external load. v is the potential difference across r and V is the potential difference across R.

Use of Potentiometer as a means of comparing potential differences



If the wire is of uniform cross-sectional area and resistivity, the <u>potential gradient k</u> ("potential difference per unit length") along the wire is uniform and given by:

$$k = \frac{V_{XY}}{l_{XY}}$$
 where l_{XY} : length of slide wire

The potential difference, V_{XJ} across a certain length *I* of the wire is directly proportional to the length *I*, i.e.,

$$V_{XJ} = kI_{XJ}$$

To find the value of V_{AB} :

Since
$$V_{AB} = V_{XJ} = kl_{XJ}$$
 and $k = \frac{V_{XY}}{l_{XY}}$,
 $V_{AB} = \frac{V_{XY}}{l_{XY}}l_{XJ}$
 $V_{AB} = \left(\frac{l_{XJ}}{l_{XY}}\right)V_{XY}$



